
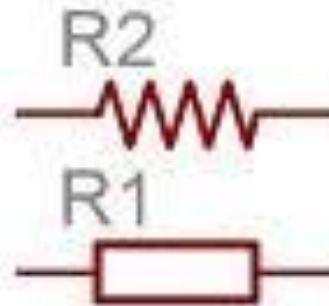



7. lecture

Part I.

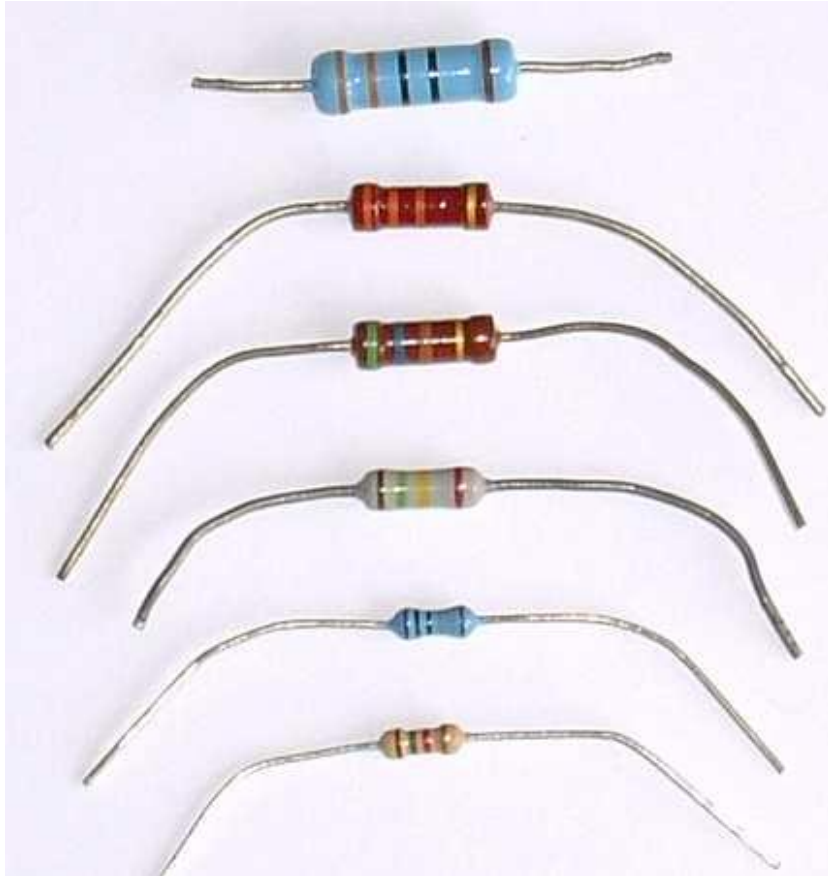

Direct current, resistors, conductivity, etc.

The CRT monitor

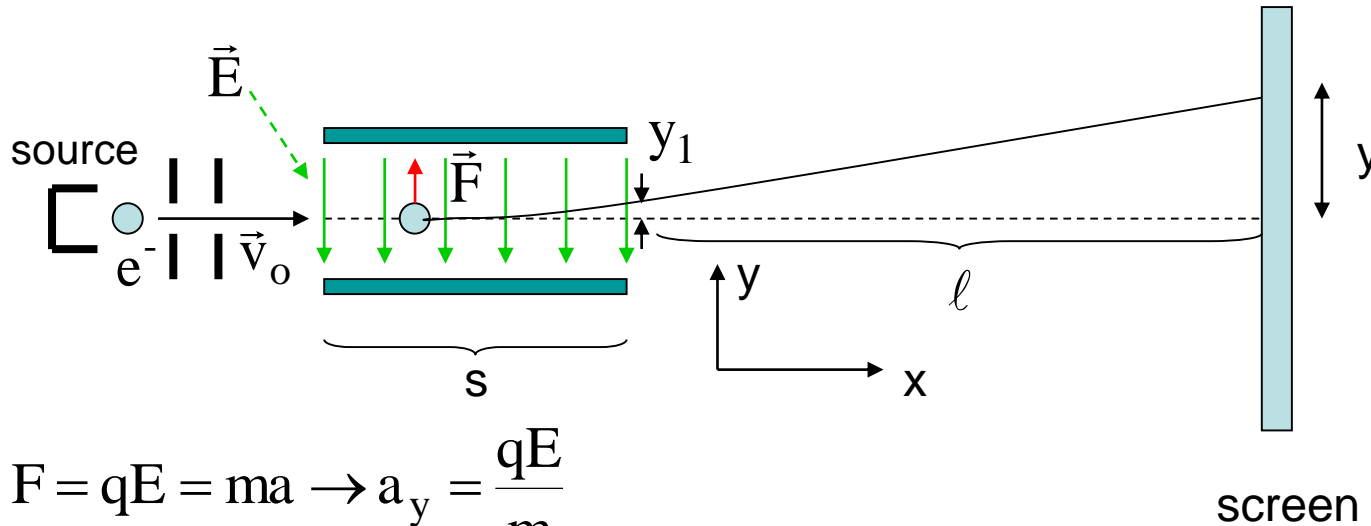

$$F = qE = ma \rightarrow a_y = \frac{qE}{m}$$

$$t_1 = \frac{s}{v_0} \rightarrow y_1 = \frac{1}{2} a_y t_1^2 = \frac{1}{2} \frac{qE}{m} \frac{s^2}{v_0^2} \quad \text{és} \quad v_y = a_y t_1 = \frac{qE}{m} \frac{s}{v_0}$$


$$t_2 = \frac{l}{v_0} \rightarrow y_2 = v_y t_2 = \frac{qE}{m} \frac{s}{v_0} \frac{l}{v_0} \quad \text{így} \quad y = y_1 + y_2 \rightarrow y \propto E$$

$$V = Ed \rightarrow y \propto V$$

V : electric potential


d : separation of plates (of capacitor)

CRT monitor

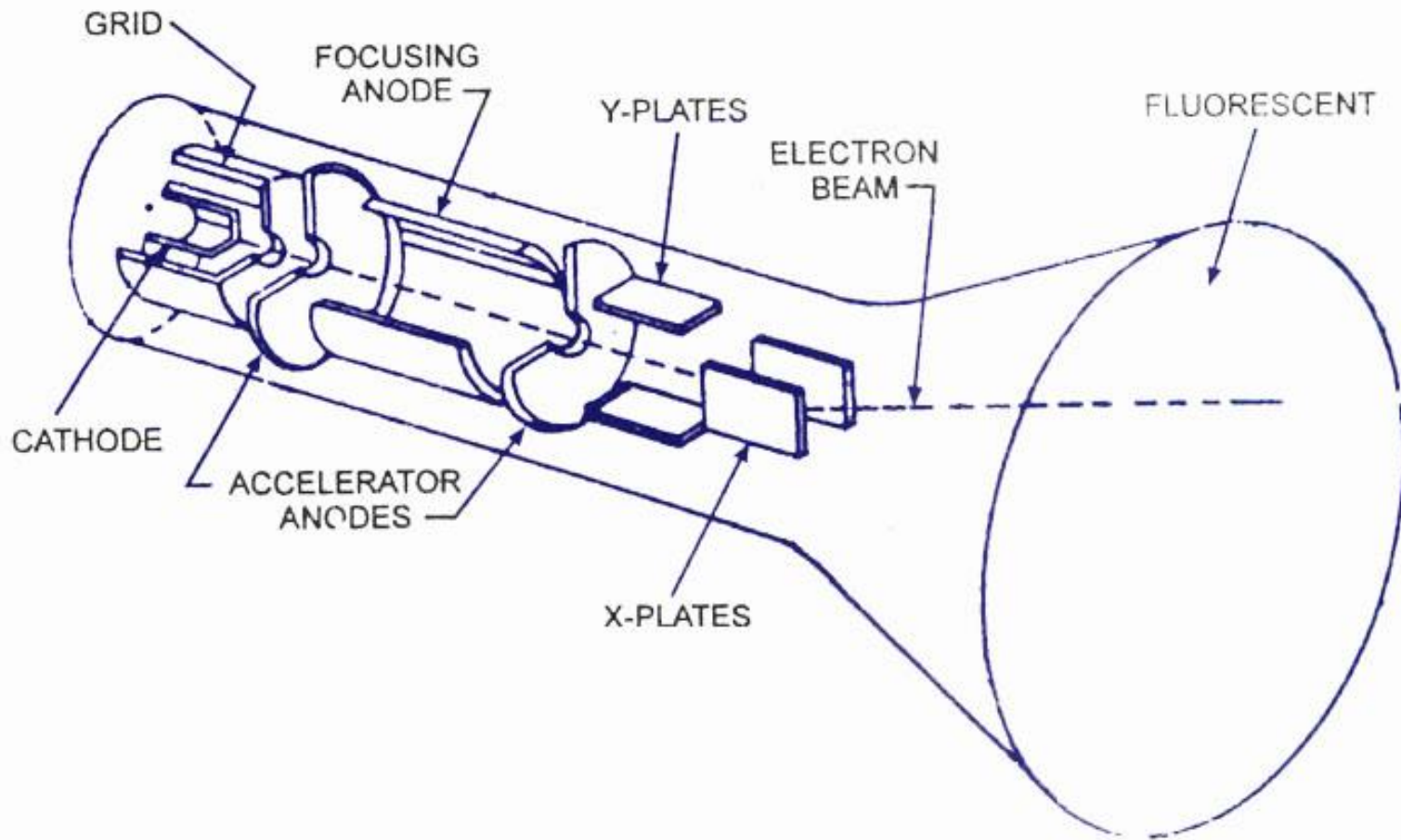

Cathode Ray Tube


Direct current, current density

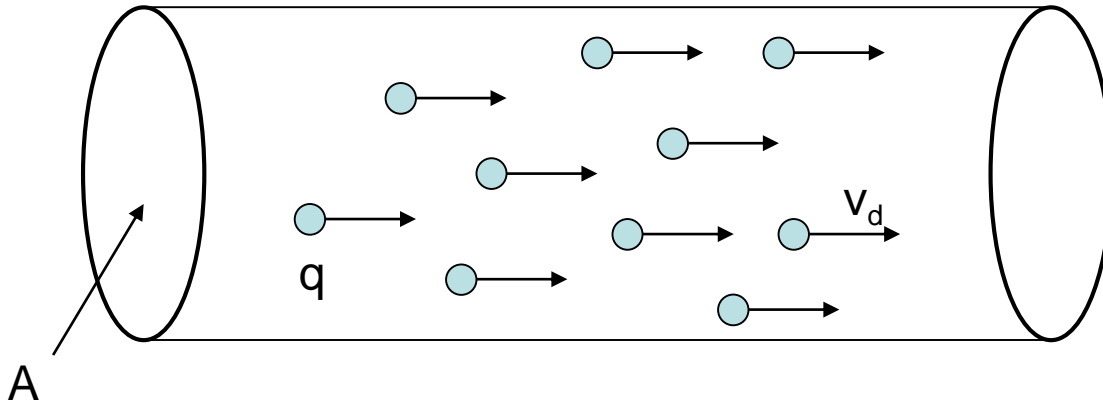

Current: $I = \frac{\Delta Q}{\Delta t}$ $\left[\frac{\text{C}}{\text{s}} = \text{A} \right]$


Current density: $J = \frac{I}{A}$ $\left[\frac{\text{A}}{\text{m}^2} \right]$

Direct current

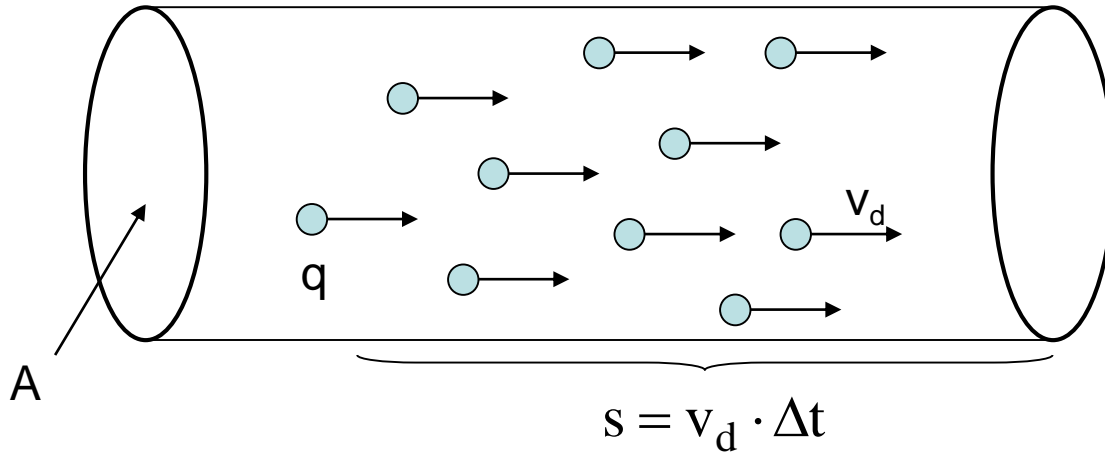

The charge of electron: q

Density of particles: n

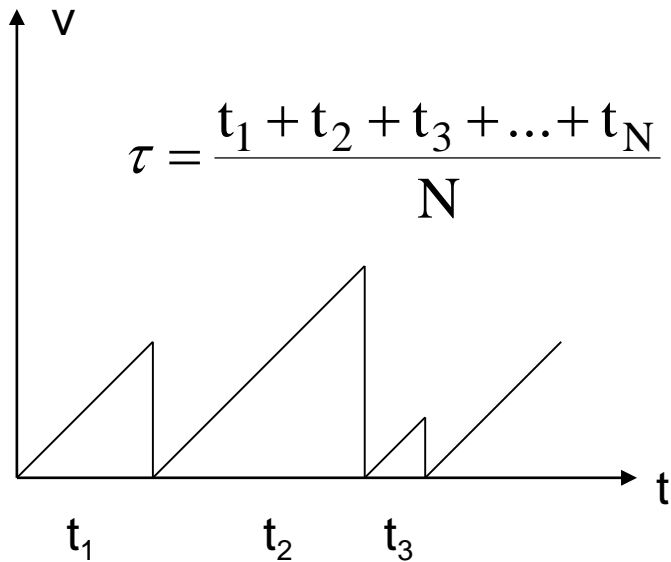


Drift speed: $v_d = \frac{qE}{m} \tau$

$$\Delta Q = Av_d \Delta t q n$$

Current: $I = \frac{\Delta Q}{\Delta t} = Av_d q n$

Current density: $J = \frac{I}{A} = v_d q n$

Direct current

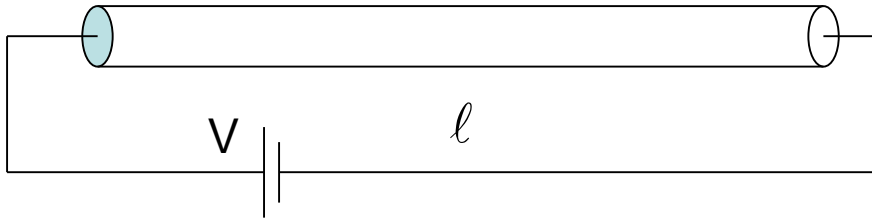

$$I = \frac{\Delta Q}{\Delta t} = A v_d q n$$

$$v_d = \frac{qE}{m} \tau$$

$$V = E l \rightarrow E = \frac{V}{l}$$

$$I = A q n \frac{qE}{m} \tau \rightarrow I = \frac{A q^2 n \tau}{m} \frac{V}{l}$$

Current density: $J = \sigma E$

$$\frac{V}{I} = \frac{m}{q n^2 \tau} \frac{l}{A} \rightarrow \boxed{\frac{V}{I} = R} \rightarrow R = \rho \frac{l}{A} \quad \text{where } \rho = \frac{m_e}{q_e n^2 \tau}$$

Ohm's law

$$\left[\frac{V}{A} = \Omega \right]$$

Resistance: ρ

Conductivity: $\sigma = \frac{1}{\rho}$

Insulators, semiconductors & metals

Substance	Resistance [Ωm]
Insulators	
Mika	$2 \cdot 10^{15}$
Glass	$2 \cdot 10^{11}$
Semiconductors	
Si (silicon)	640
Ge (germanium)	0,46
Conductors	
Aluminum	$2.8 \cdot 10^{-8}$
Copper	$1.7 \cdot 10^{-8}$
Gold	$2.4 \cdot 10^{-8}$
Iron	$10 \cdot 10^{-8}$


Resistance depends on temperature

$$\rho = \rho_o (1 + \alpha(T - T_o))$$

$$\alpha \propto 10^{-3} \frac{1}{^{\circ}C}$$

(electric thermometer)

Colour code: 

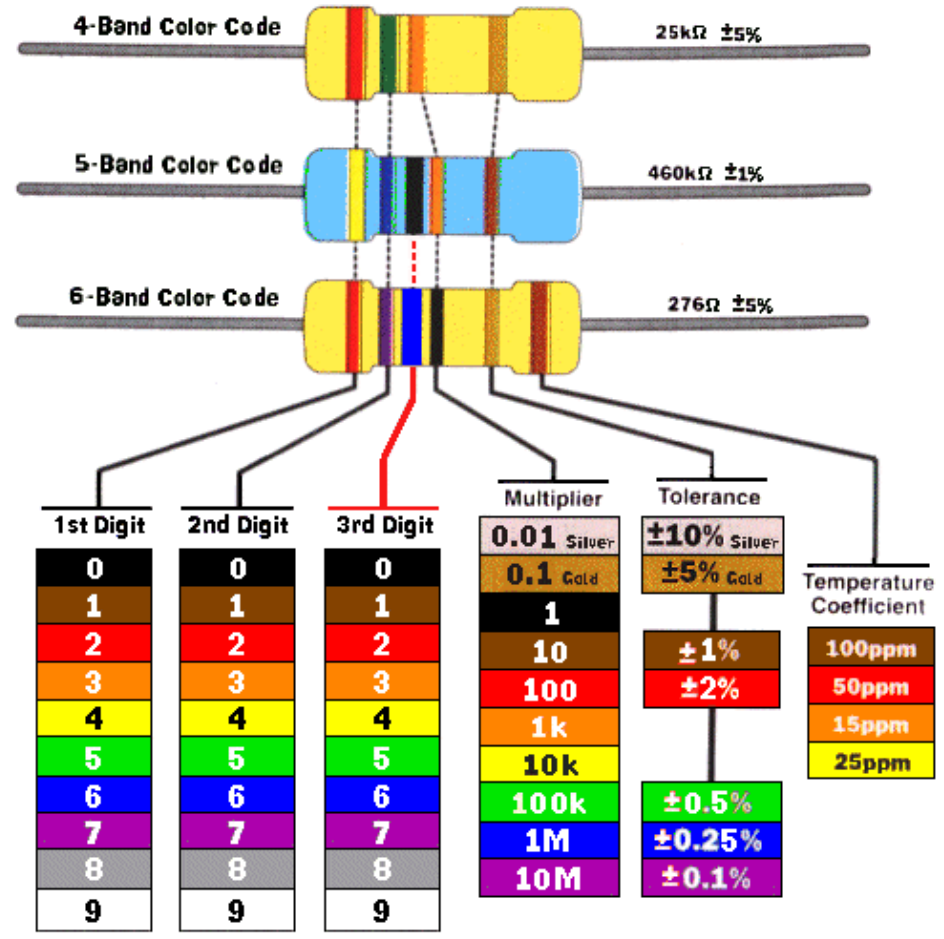


Joule's law

$$dW = Vdq$$



$$P = \frac{dW}{dt} = V \frac{dq}{dt} = VI$$
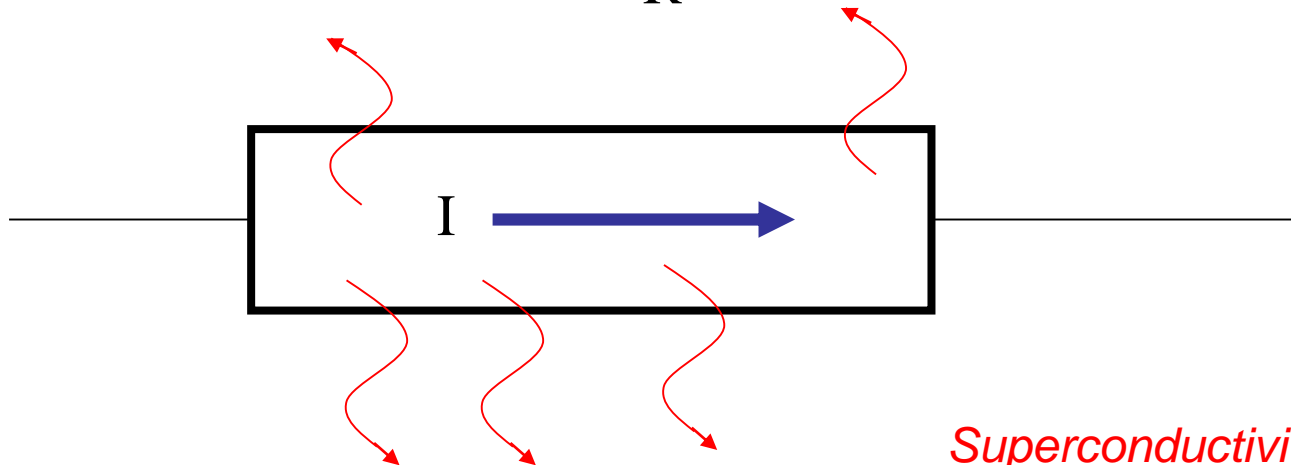
$$V = IR \rightarrow P = VI = RI^2 = \frac{V^2}{R}$$




Superconductivity???

Part II.

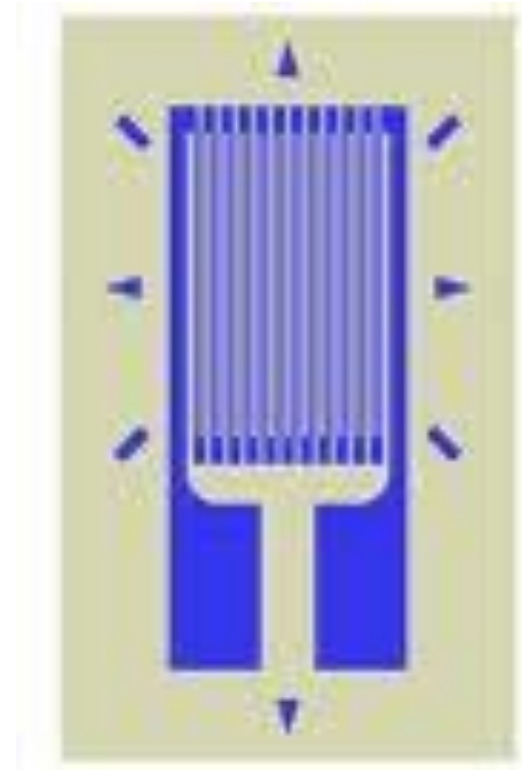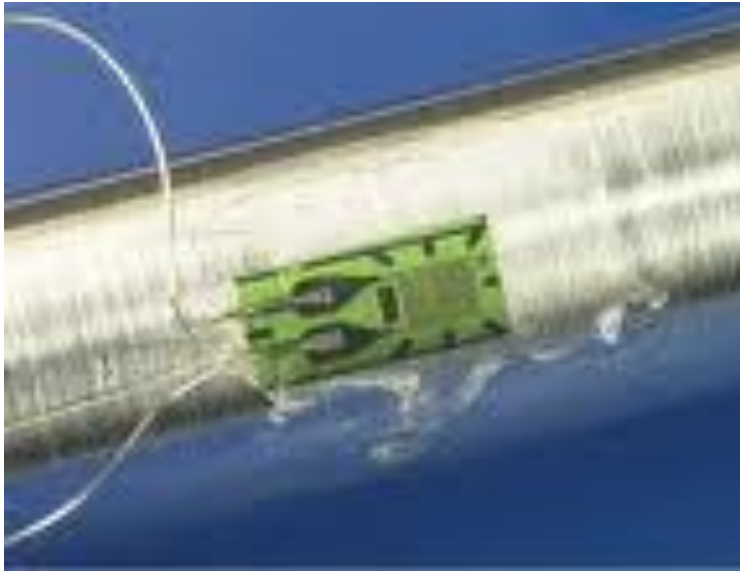

Direct current circuits

Series combination of resistors:

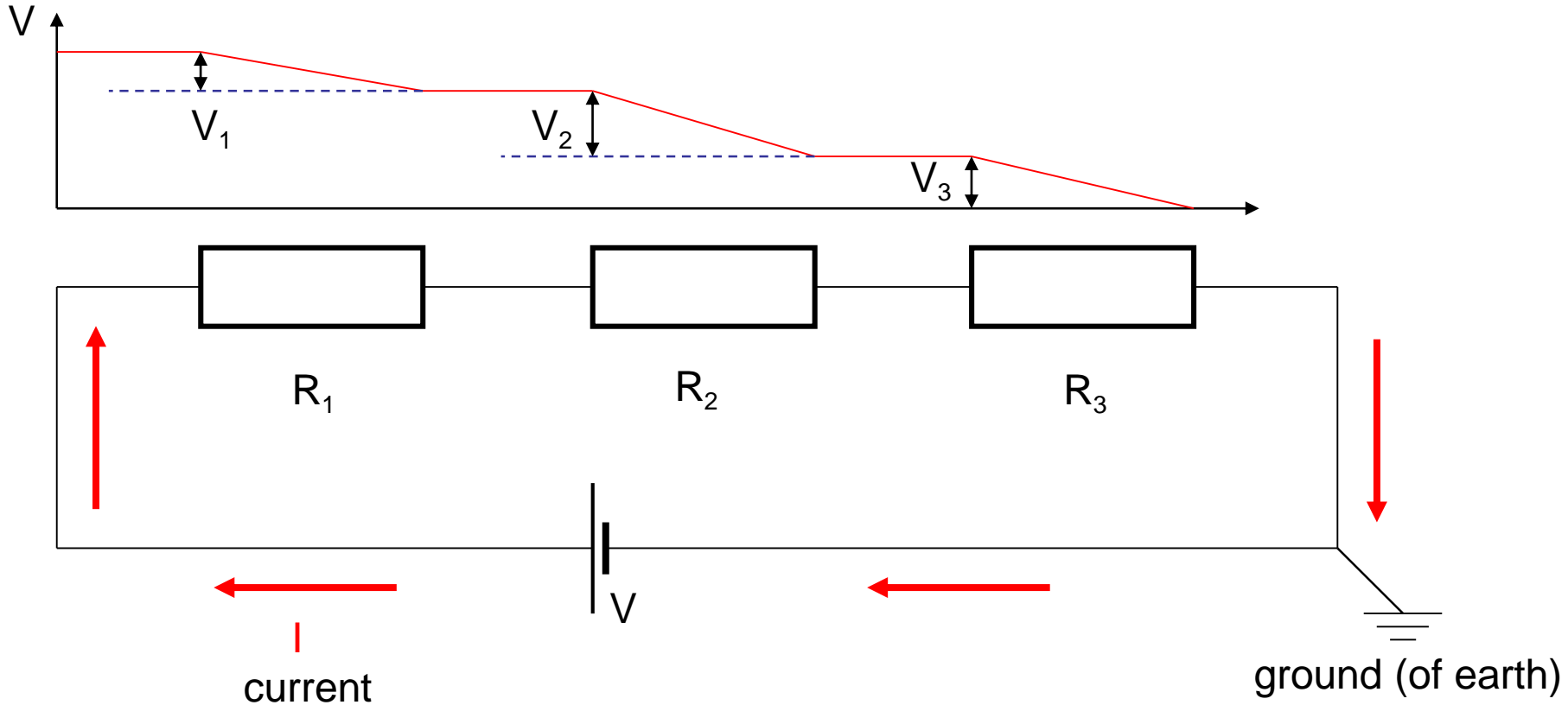

$$\left. \begin{aligned} V &= V_1 + V_2 + V_3 \\ V_1 &= IR_1 \\ V_2 &= IR_2 \\ V_3 &= IR_3 \end{aligned} \right\}$$

$$V = IR_e$$

$$IR_e = IR_1 + IR_2 + IR_3$$

$$R_e = R_1 + R_2 + R_3$$

$$R_e = \sum_i R_i$$

Parallel combination of resistors:


$$I = I_1 + I_2 + I_3$$

$$I_1 = \frac{V}{R_1}$$

$$I_2 = \frac{V}{R_2}$$

$$I_3 = \frac{V}{R_3}$$

$$I = \frac{V}{R_e}$$

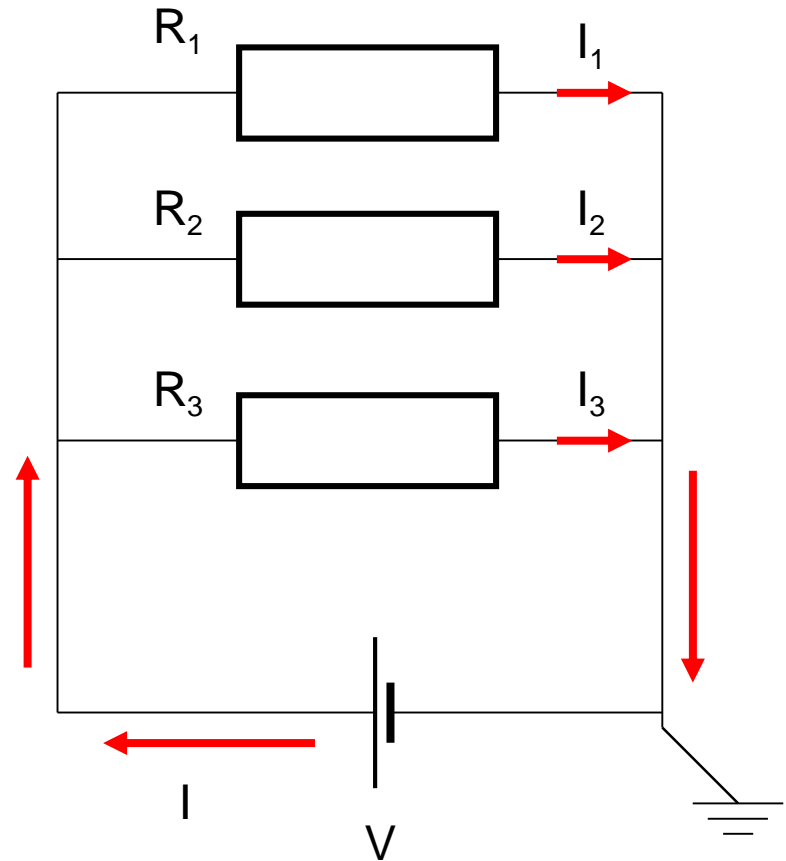


$$\frac{V}{R_e} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \longrightarrow \frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_e} = \sum_i \frac{1}{R_i}$$

Kirchoff's rules


1. Junction rule

$$I_1 + I_2 + I_3 - I_4 - I_5 = 0$$

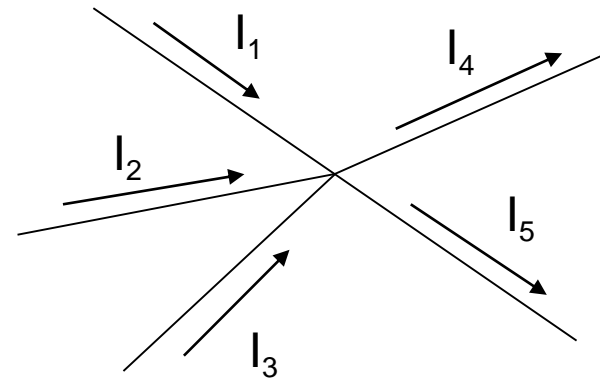


2. Loop rule

$$V_1 - I_1R_1 - I_2R_2 = 0$$

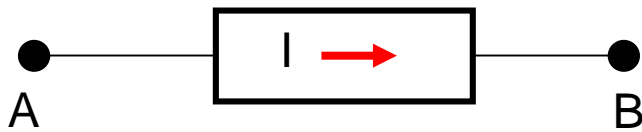


$$V_{AB} = -IR$$

$$V_{BA} = +IR$$

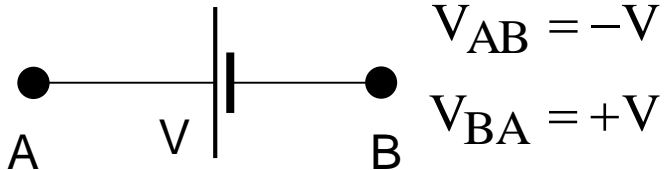


$$V_{AB} = -V$$

$$V_{BA} = +V$$

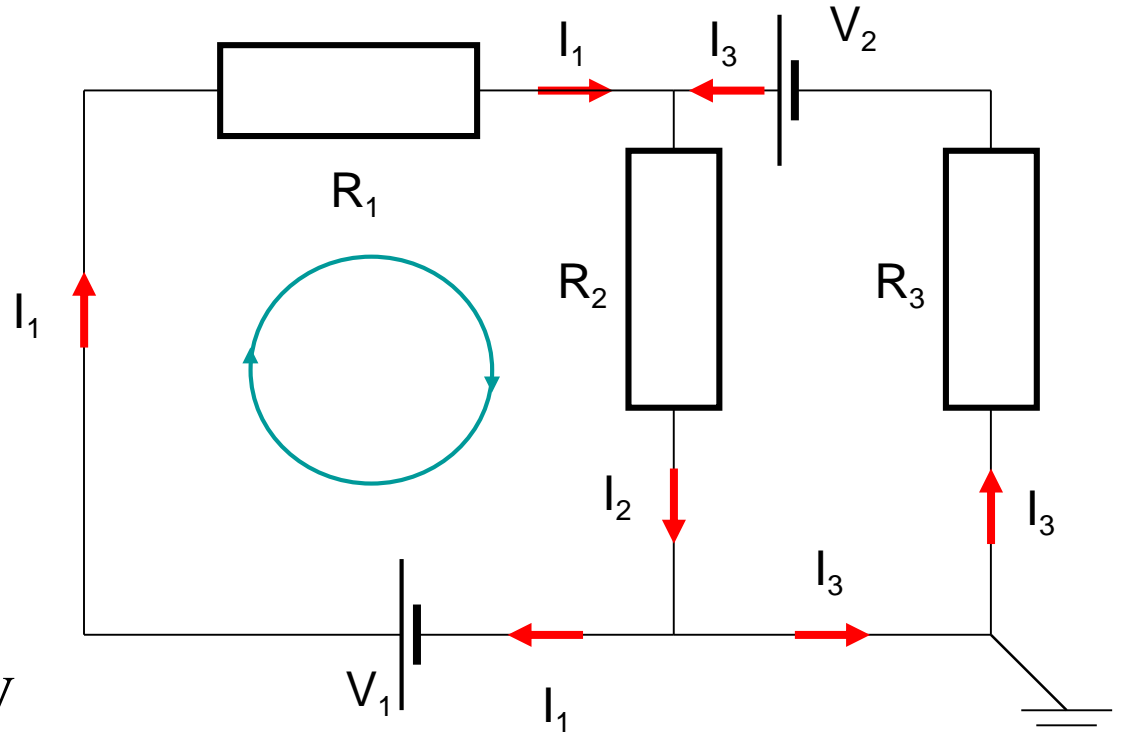

Wheatstone-bridge

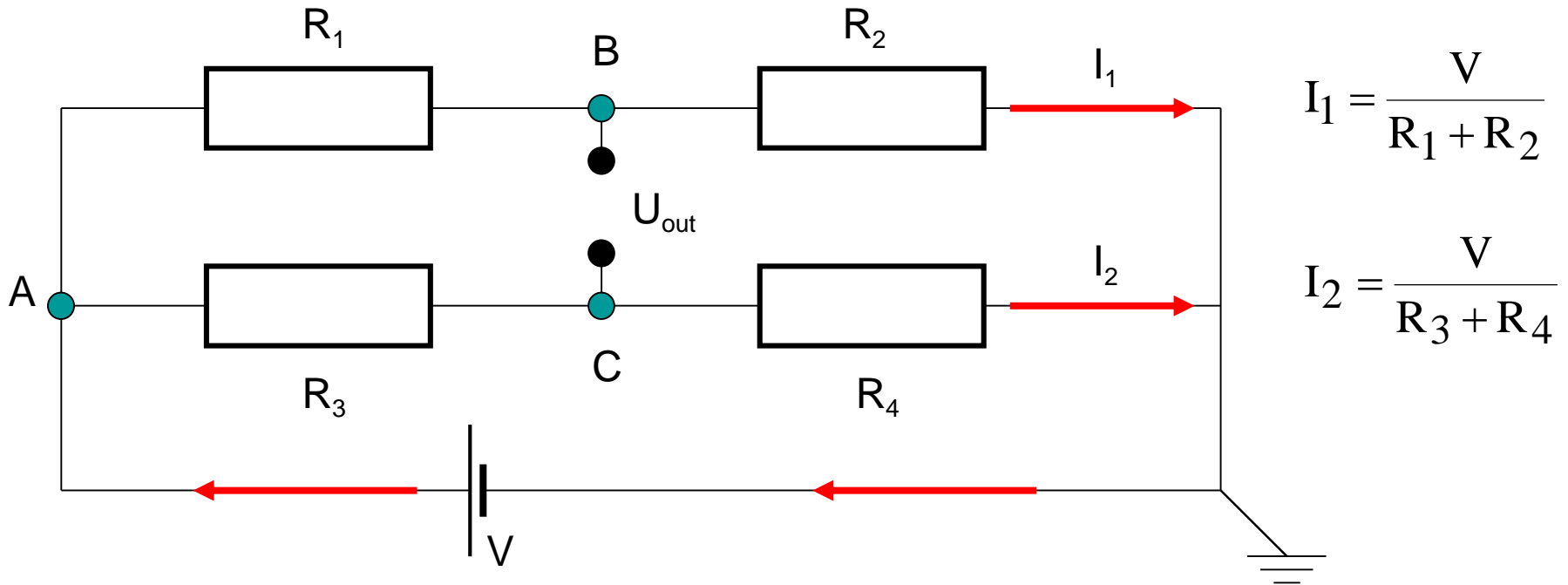


$$I_1 = \frac{V}{R_1 + R_2}$$

$$I_2 = \frac{V}{R_3 + R_4}$$

$$V_{BA} = I_1 R_1 = \frac{V}{R_1 + R_2} R_1 \quad V_{CA} = I_2 R_3 = \frac{V}{R_3 + R_4} R_3 \quad U_{out} = V_{BA} - V_{CA}$$

$$U_{out} = \frac{V}{R_1 + R_2} R_1 - \frac{V}{R_3 + R_4} R_3 = V \frac{R_1(R_3 + R_4) - R_3(R_1 + R_2)}{(R_1 + R_2)(R_3 + R_4)} = V \frac{R_1 R_4 - R_3 R_2}{(R_1 + R_2)(R_3 + R_4)}$$

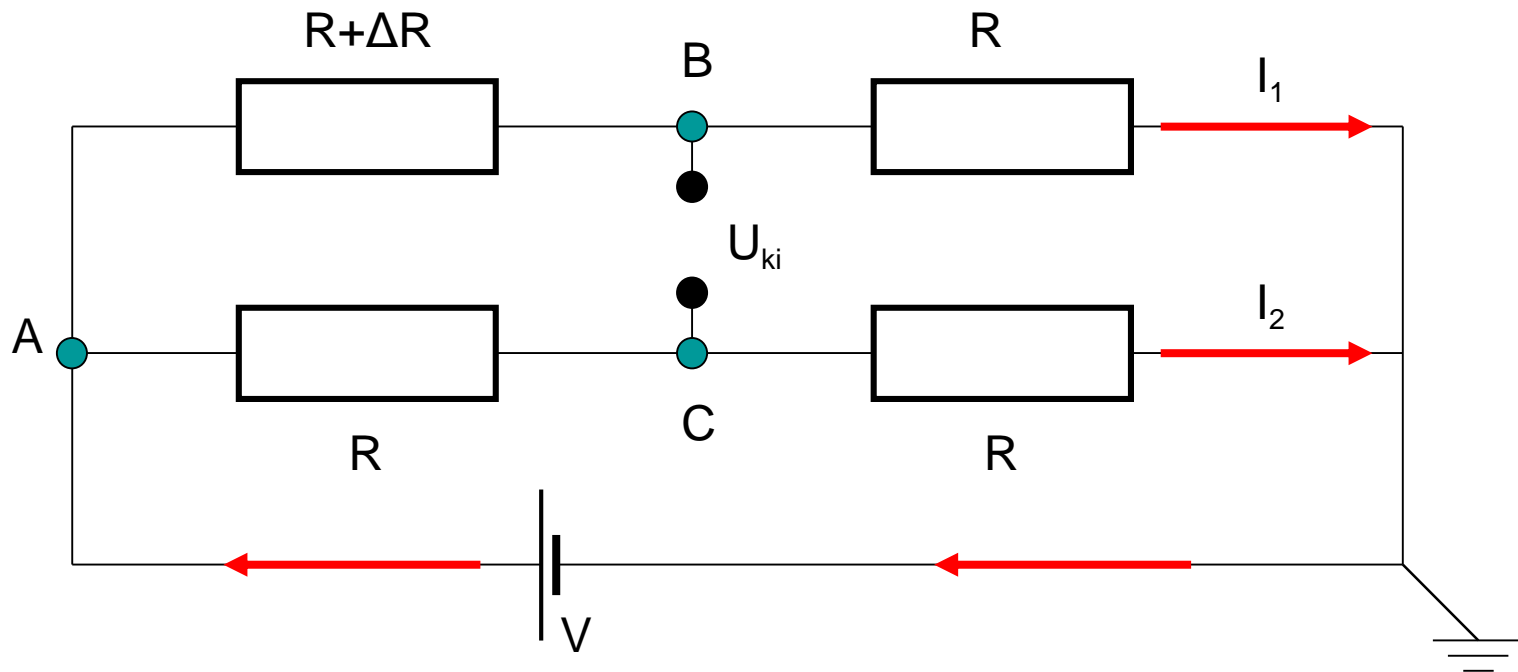The measurement of change in resistance with Wheatstone-bridge



$$U_{ki} = V \frac{(R + \Delta R)R - RR}{(2R + \Delta R)(2R)} = \frac{V \Delta R}{4 R}$$